

EE-238

Homework 5

ID : 011491649

Name : Ju-Wei Huang


Due Date : 05/23/2017

1- For the Buck converter shown below, it is desired to control the output voltage to be 15 V

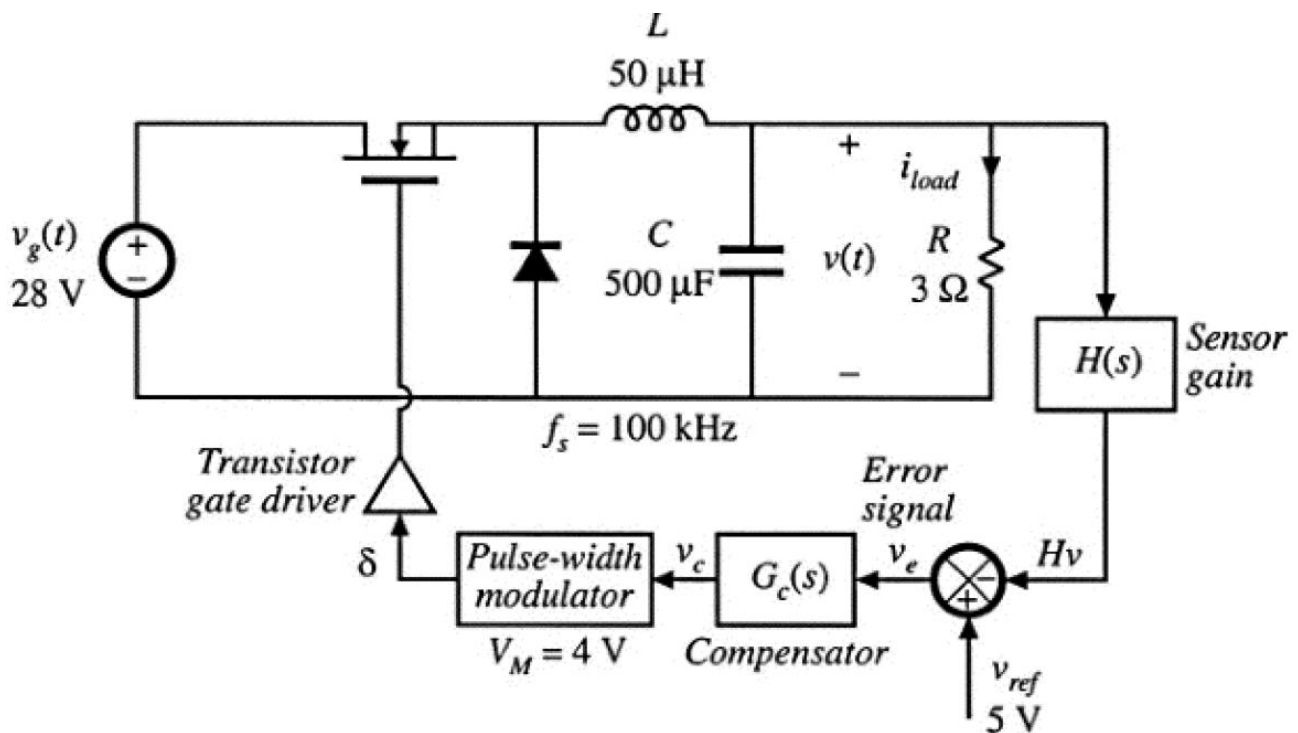- a) What should $H(s)$ be equal to and why?
- b) What is the expected system duty ratio assuming ideal characteristics?
- c) Find $G_v(s)$ and $G_d(s)$ of the given system.
- d) Find the natural frequency (f), the quality factor (Q) and the DC gain for both of the transfer functions.
- e) Plot the Bode plots of both of the transfer functions.
- f) Assuming that the only disturbance in the system is the input voltage variations, draw the control block diagram of the system.
- g) Find the loop gain transfer function $T(s)$ with $G_c(s) = 1$.
- h) Draw the Bode Plot of the $T(s)$.
- i) What is the difference between $G_d(s)$ and $T(s)$ bode plots.
- j) Find the system crossover frequency and phase margin.
- k) Simulate the converter in a circuit simulation software using the same parameters given and shown (including the reference voltage, the unity compensator, the V_m value, etc.). Show the system output voltage and inductor current from your circuit simulation file (while applying the feedback control).
- l) Show the system response for a small change in the reference voltage and a small change in the input voltage from both the simulated circuit and your $T(s)$ model with $G_c(s) = 1$ (while applying the feedback control).
- m) Design a PD compensator to attain a crossover frequency of 5 kHz and a phase margin of 52 degrees.
- n) Write the PD compensator transfer function and draw its bode plot.
- o) Draw the bode plot of the $T(s)$ where $G_c(s)$ is the PD compensator and show if you were able to meet the desired control requirements (crossover frequency and phase margin).
- p) Show the system response for a small change in the reference voltage and a small change in the input voltage from both the simulated circuit and your $T(s)$ model with $G_c(s)$ being the PD compensator transfer function (while applying the feedback control).
- q) Enhance the performance of your PD controller through the addition of an inverted zero (PI controller) so that the transfer function become a PID controller in order to increase the system low frequency gain. Choose the inverted zero frequency to be one tenth of the


crossover frequency used in m).

- r) Write the PID compensator transfer function and draw its bode plot.
- s) Draw the bode plot of the $T(s)$ where $G_c(s)$ is the PID compensator and show if you are still able to meet the desired control requirements (crossover frequency, phase margin and DC gain).
- t) Show the system response for a small change in the reference voltage and a small change in the input voltage from both the simulated circuit and your $T(s)$ model with $G_c(s)$ being the PID compensator transfer function (while applying the feedback control).
- u) Comment on the results in l), p) & t).



Q1

Buck

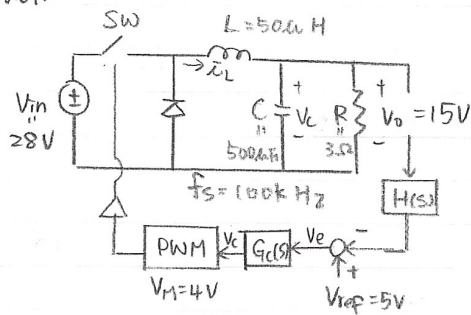


$$G_{vd}(s) = \frac{G_{do} (1 - s/\omega_z)}{(1 + \frac{s}{Q\omega_0} + (\frac{s}{\omega_0})^2)}$$

$$\begin{aligned} G_{go} &= D \\ G_{do} &= V_o/D \\ \omega_0 &= 1/\sqrt{LC} \\ Q &= R\sqrt{C/L} \\ \omega_z &= \infty \end{aligned}$$

$$G_{vg}(s) = \frac{G_{go}}{(1 + \frac{s}{Q\omega_0} + (\frac{s}{\omega_0})^2)}$$
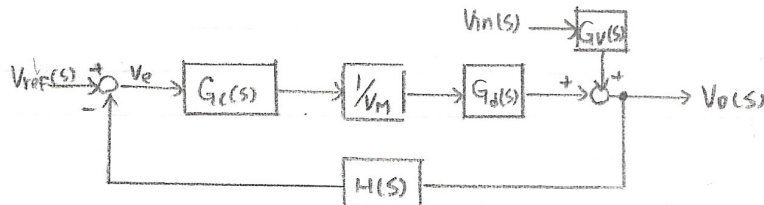
$$V_o(s) = V_{ref}(s) * \frac{1}{H(s)} * \frac{T(s)}{1 + T(s)} + V_{in}(s) * \frac{G_v(s)}{1 + T(s)}$$



$$T(s) = H(s) G_c(s) G_d(s) * \frac{1}{V_m}$$

a)

$$\text{if } \|T\| \gg 1 \Rightarrow \frac{\hat{V}_o}{\hat{V}_{ref}} = \frac{1}{H(s)} \Rightarrow H(s) = \frac{\hat{V}_{ref}}{\hat{V}_o} = \frac{1}{3}$$

this is the value we want in steady state.

b)

$$\frac{V_o}{V_{in}} = D = \frac{15}{28} = \underline{\underline{0.536}}$$

c)

$$G_{go} = 0.536 \quad G_{do} = 28 \quad \omega_0 = \frac{1}{1.58 \times 10^{-4}} = 6324.56 \quad Q = 3\sqrt{10} = 9.49$$

$$G_{vg} = \frac{0.536}{1 + \frac{s}{60020.07} + (\frac{s}{6324})^2} = \frac{0.536}{1 + 1.67 \times 10^{-5} s + 2.5 \times 10^{-8} s^2}$$



$$G_{vd} = \frac{28}{1 + 1.67 \times 10^{-5} s + 2.5 \times 10^{-8} s^2}$$

d)

$$\begin{aligned} f_0 &= \frac{\omega_0}{2\pi} = \underline{\underline{1007 \text{ Hz}}} \\ Q_0 &= R\sqrt{C/L} = \underline{\underline{9.49}} \end{aligned}$$

$$\underline{\underline{G_{go} = 0.536}}$$

$$\underline{\underline{G_{do} = 28}}$$

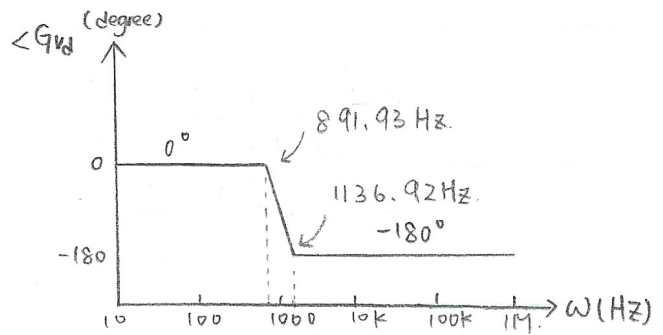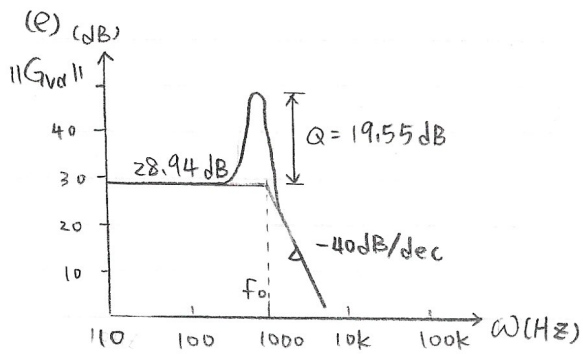



$$G_{d0} = 28 \rightarrow 28.94 \text{ dB}$$

$$Q = 9.49 \rightarrow 19.55 \text{ dB}$$

$$f_o = 1007 \text{ Hz}$$

$$10^{1/2 Q} f_o = 10^{0.0527} f_o = 1136.92$$


$$10^{-1/2 Q} f_o = 891.93 \text{ Hz}$$

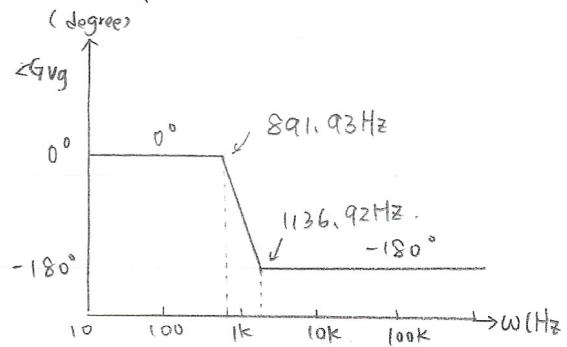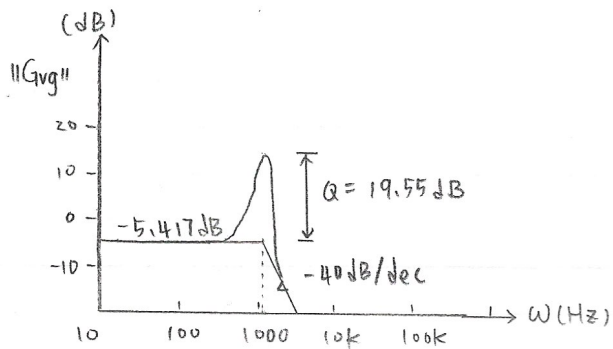

$$G_{g0} = 0.536 = -5.417 \text{ dB}$$

$$Q = 19.55 \text{ dB}$$


(f).

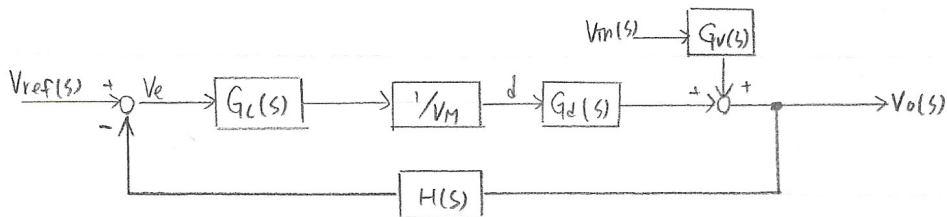


(g)

$$T(s) = H(s) G_c(s) G_d(s) \frac{1}{V_m} = \frac{1}{3} \times 1 \times \frac{28}{1 + 1.67 \times 10^{-5} s + 2.15 \times 10^{-8} s^2} \times \frac{1}{4}$$
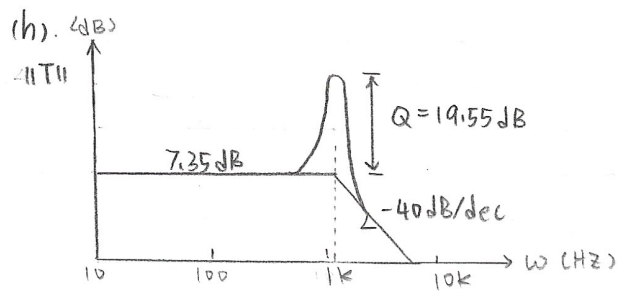
$$= \frac{2.3}{1 + 1.67 \times 10^{-5} s + 2.15 \times 10^{-8} s^2}$$


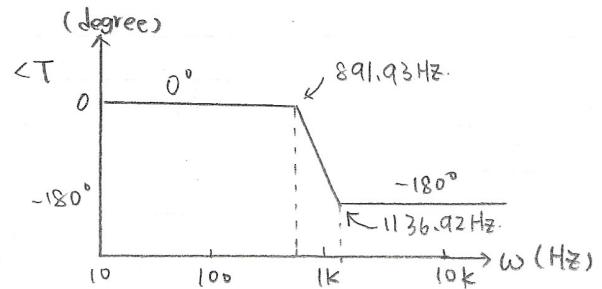
$$T_0 = 2.33 \rightarrow 7.35 \text{ dB}$$



(i)

The Bode plots of $G_d(s)$ and $T(s)$ are really familiar.
The difference between them is on the magnitude part.
The DC gain is different.

(j)

By using MATLAB function $[G_m, P_m, W_{gm}, W_{pm}]$
we can get G_d 's crossover frequency = $3.19 \times 10^4 = \underline{31900 \text{ Hz}}$
phase margin = 1.09 dB

T 's crossover frequency = $1.0803 \times 10^4 = \underline{10803 \text{ Hz}}$
phase margin = 4.4346 dB

```
>> Gd = tf ([28] , [2.85*10^-8 1.67*10^-5 1])
```

Gd =

$$\frac{28}{2.85e-08 s^2 + 1.67e-05 s + 1}$$

Continuous-time transfer function.

```
>> T = tf ([28/12] , [2.85*10^-8 1.67*10^-5 1])
```

T =

$$\frac{2.333}{2.85e-08 s^2 + 1.67e-05 s + 1}$$

Continuous-time transfer function.

```
>> [Gm,Pm,Wgm,Wpm] = margin(Gd)
```

Gm =

Inf

Pm =

1.0900



Wgm =

Inf

Wpm =


3.1898e+04

(k)

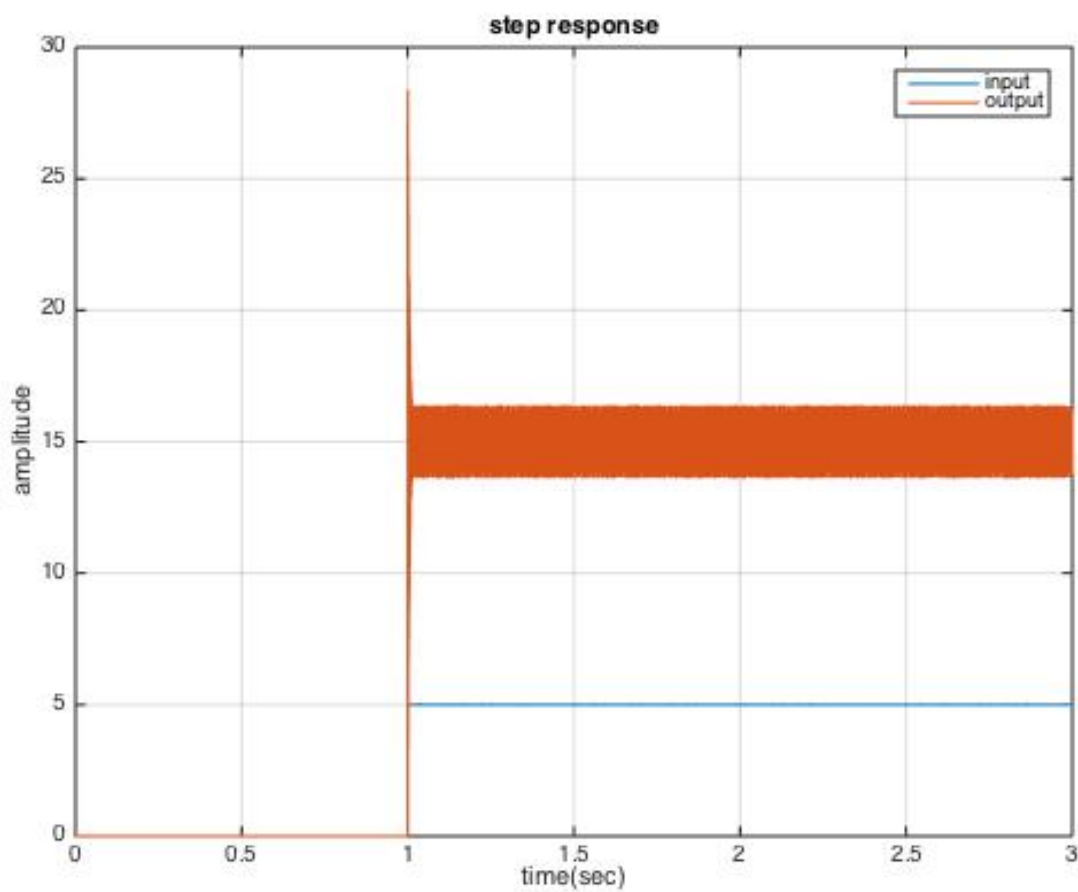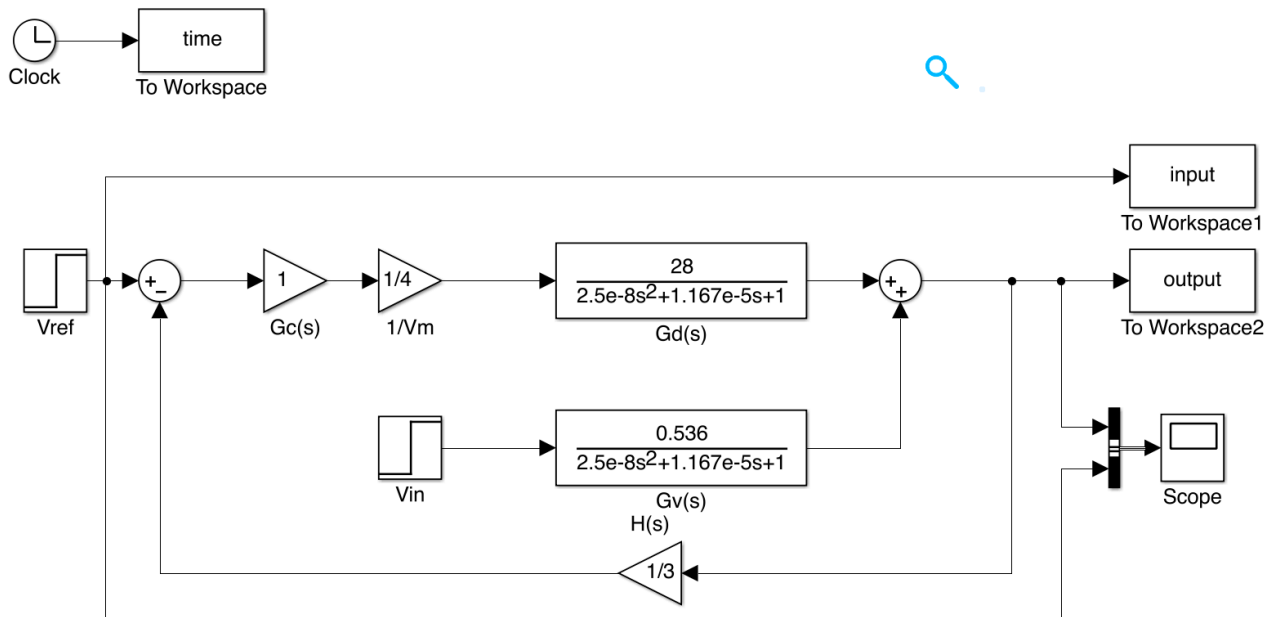

the blue line is V_{ref} not V_{in}

(l)

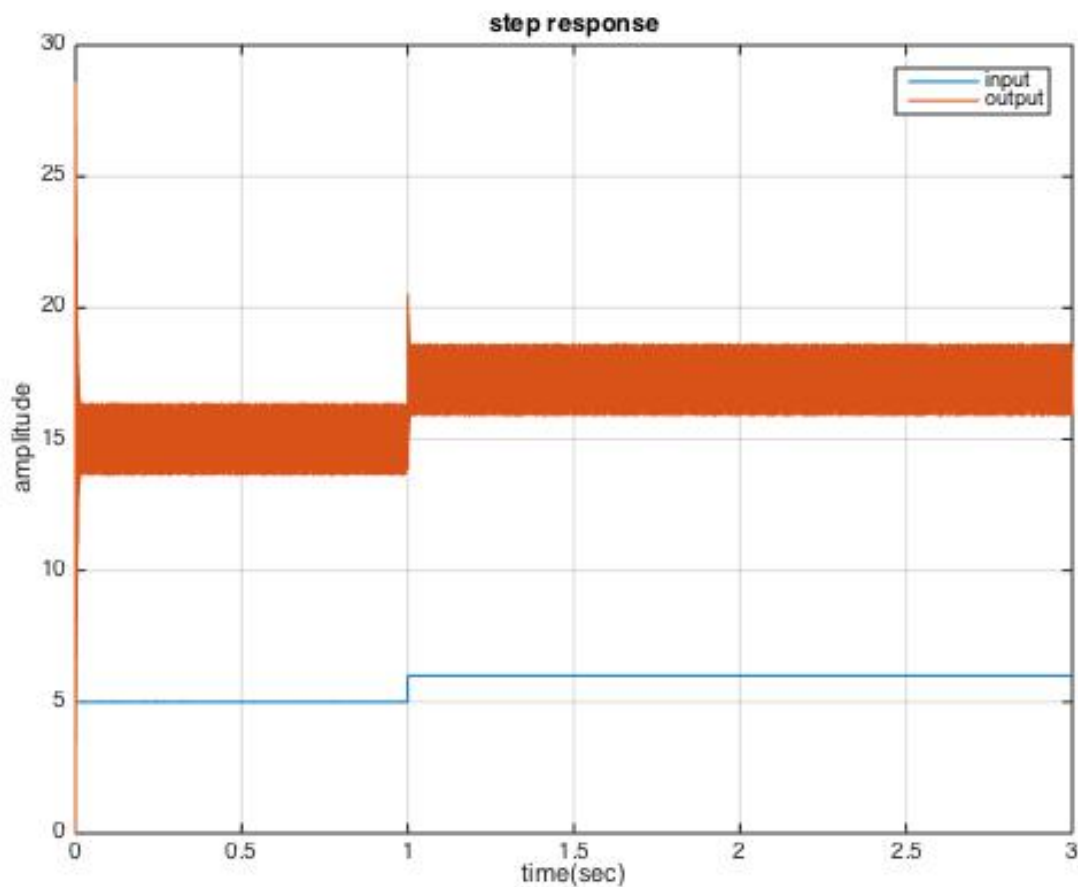the blue line is V_{ref} not V_{in} 

(m)

PD compensator $\Rightarrow f_c = 5 \text{ kHz}$, $\Phi_m = 52^\circ$

$$G_c(s) = G_{co} \frac{(1 + s/\omega_z)}{(1 + s/\omega_p)}$$

$$f_z = f_c \sqrt{\frac{1 - \sin(\theta)}{1 + \sin(\theta)}} = 5 \text{ k} \sqrt{\frac{0.212}{1.788}} = 3739.25 \text{ Hz} \Rightarrow \omega_z = 23494.4$$

$$f_p = f_c \sqrt{\frac{1 + \sin(\theta)}{1 - \sin(\theta)}} = 5 \text{ k} \sqrt{\frac{1.788}{0.212}} = 14521.05 \text{ Hz} \Rightarrow \omega_p = 91238.45$$


Assume that I want the magnitude of the compensator gain at f_c is unity.

$$\Rightarrow G_{co} = \sqrt{\frac{f_z}{f_p}} = 0.507$$

$$\Rightarrow G_c(s) = \frac{0.507(1 + 4.256 \times 10^{-5}s)}{(1 + 1.096 \times 10^{-5}s)}$$

(h.)


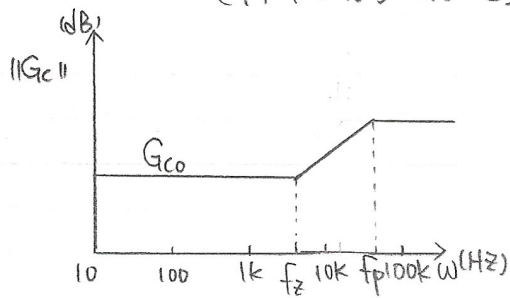
$$G_c(s) = \frac{0.507 (1 + 4.256 \times 10^{-5} s)}{(1 + 1.0965 \times 10^{-5} s)}$$



$$f_z = 3.74 \text{ kHz}$$

$$f_p = 14.5 \text{ kHz}$$
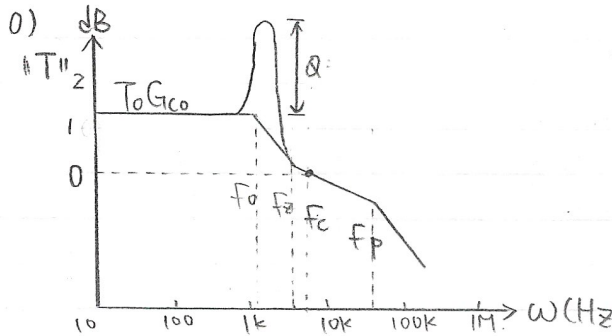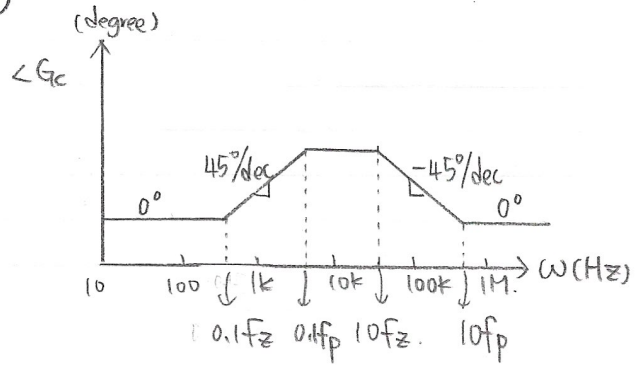
$$G_{co} = 0.507 \Rightarrow -5.9 \text{ dB}$$



$$T_0 G_{co} = 1.181 \Rightarrow 1.445 \text{ dB}$$


$$f_0 = 1007 \text{ Hz}$$

$$f_z = 3739 \text{ Hz}$$

$$f_p = 14521 \text{ Hz}$$

$$f_c = 5 \text{ kHz}$$

$$Q = 19.55 \text{ dB}$$

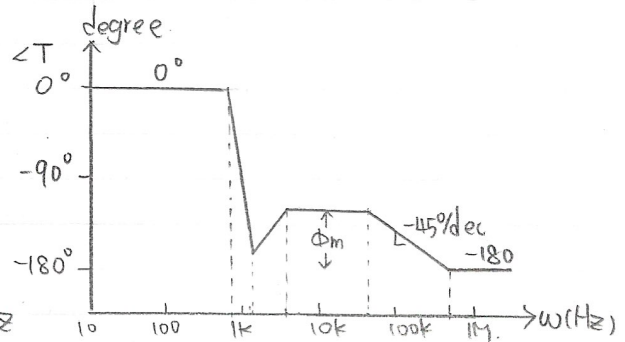


$$10^3 f_0 = 892 \text{ Hz}$$

$$10^2 f_0 = 1137 \text{ Hz}$$

S.H.W.L.

(p)

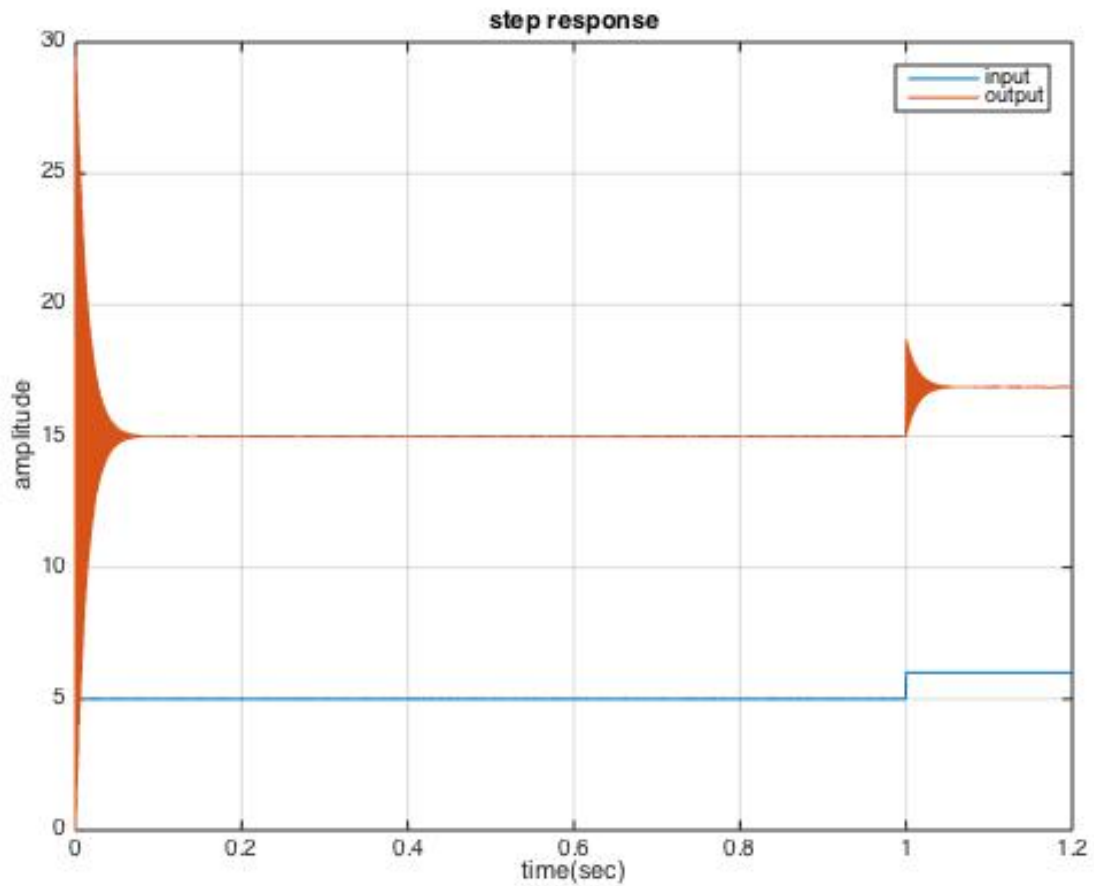the blue line is V_{ref} not V_{in} 

(q)

$$\text{PI compensator: } G_{c\infty} \left(1 + \frac{\omega_L}{s}\right) = (1 + 3141.6 \times s^{-1})$$

$$f_L = 0.1 f_c = 5k \times 0.1 = 500 \text{ Hz}$$



$$\Rightarrow \omega_L = 3141.6 \text{ Hz}$$

$$\text{Assume } G_{c\infty} = 1$$

(r)

$$\text{PID compensator: } G_{c0} G_{c\infty} \frac{(1 + \omega_L/s)(1 + s/\omega_z)}{(1 + s/\omega_p)}$$
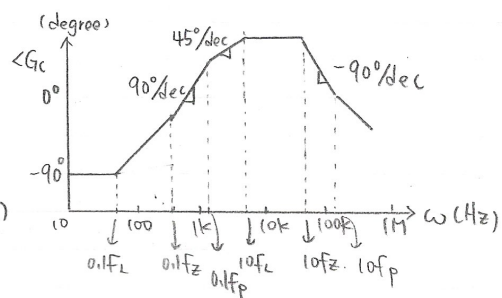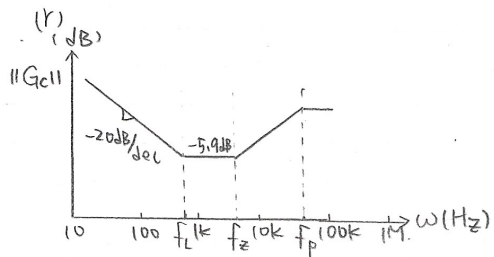
$$= \frac{0.507 (1 + 3141.6/s)(1 + 4.256 \times 10^{-5} s)}{(1 + 1.0965 \times 10^{-5} s)}$$



$$G_{c0} G_{c\infty} = 0.507 \rightarrow -5.9 \text{ dB}$$

$$f_L = 500 \text{ Hz}$$


$$f_z = 3739 \text{ Hz}$$

$$f_p = 14521 \text{ Hz}$$


$$f_c = 5k \text{ Hz}$$



(s)

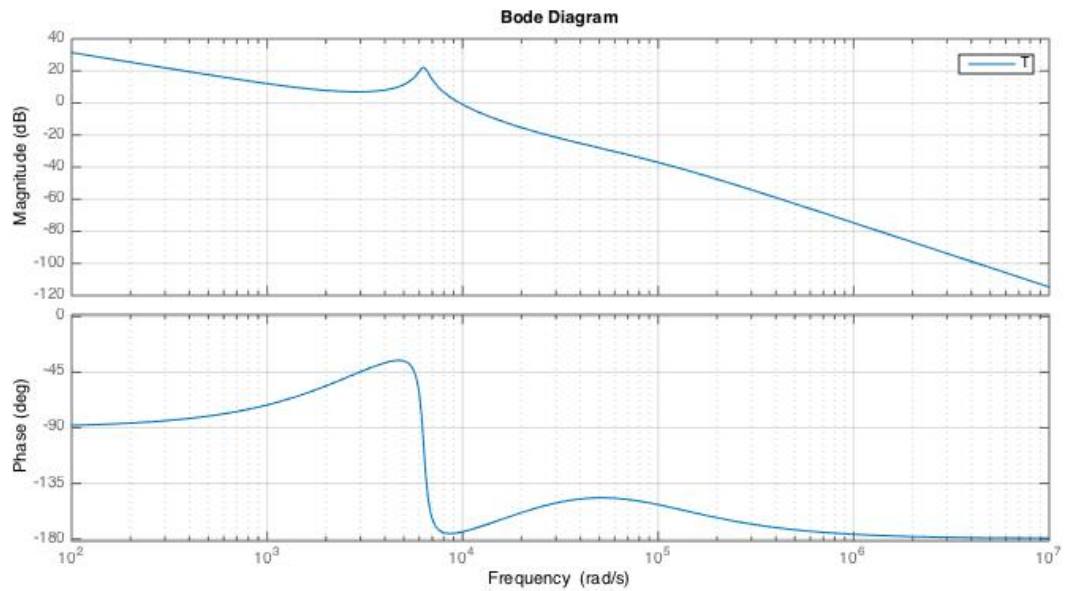
```
>> Gd=tf([28], [2.5e-8 1.67e-5 1]);
>> Gc=tf([0.507*4.26e-5 0.507*(1+0.134) 0.507*3141.6],[1.096e-5 1 0]);
>> H=1/3;
>> Vm=4;
>> T=H*Gc*Gd/Vm;
>> bode(T)
```



(t)

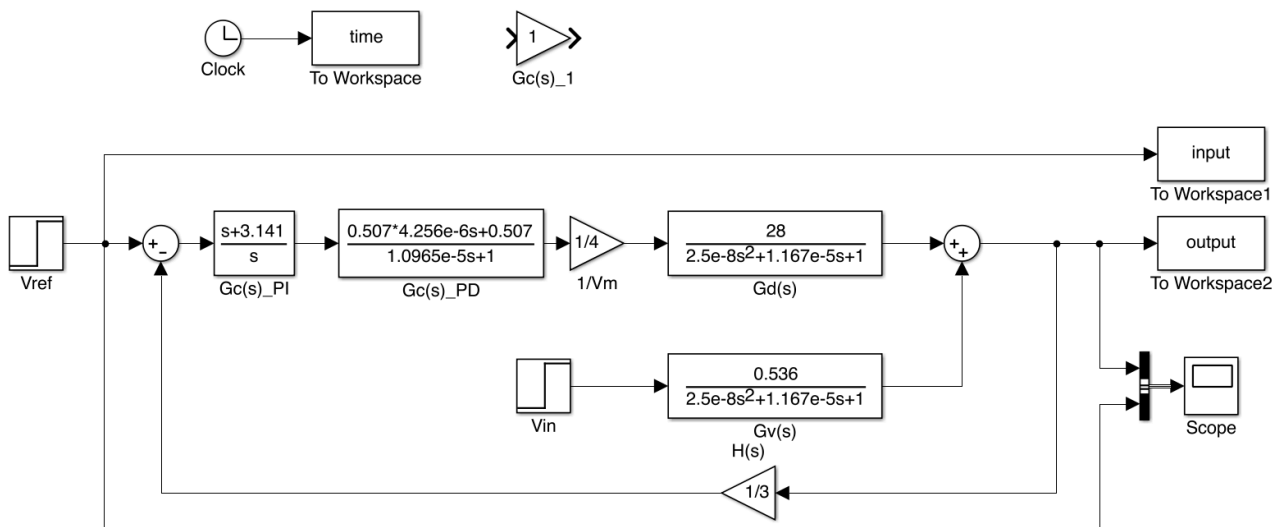

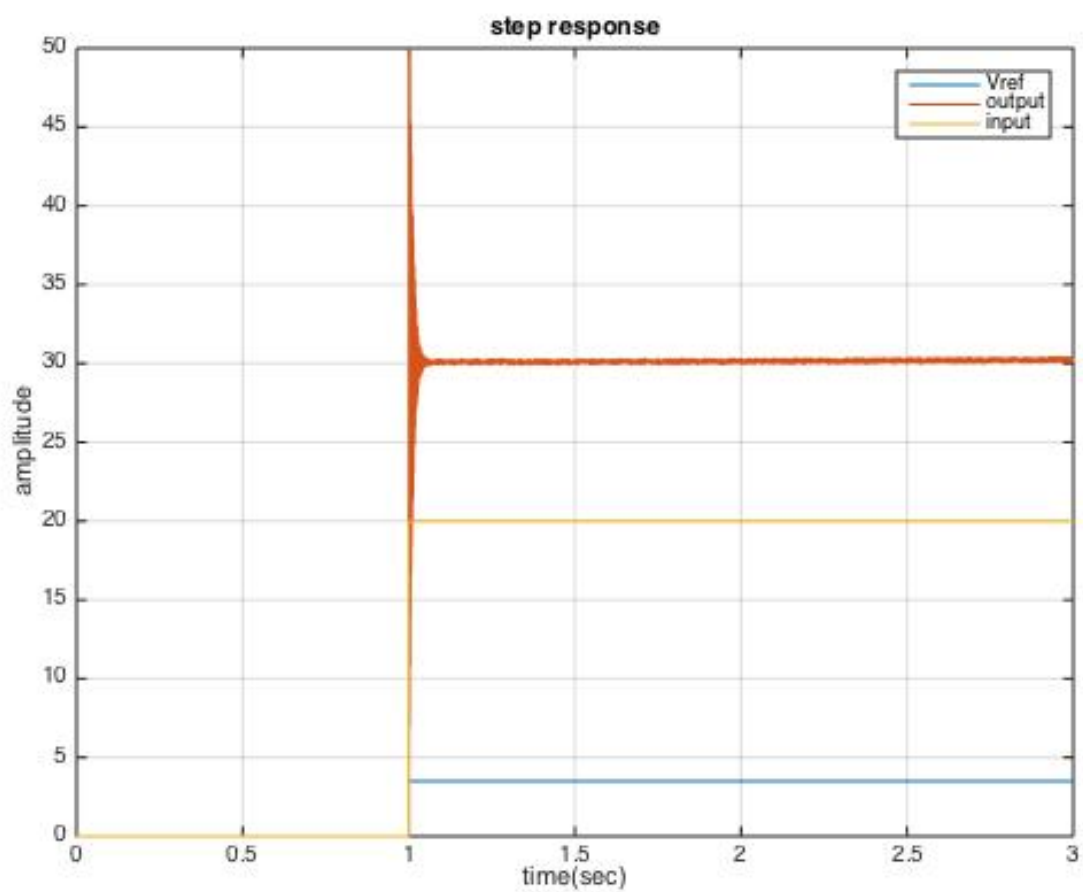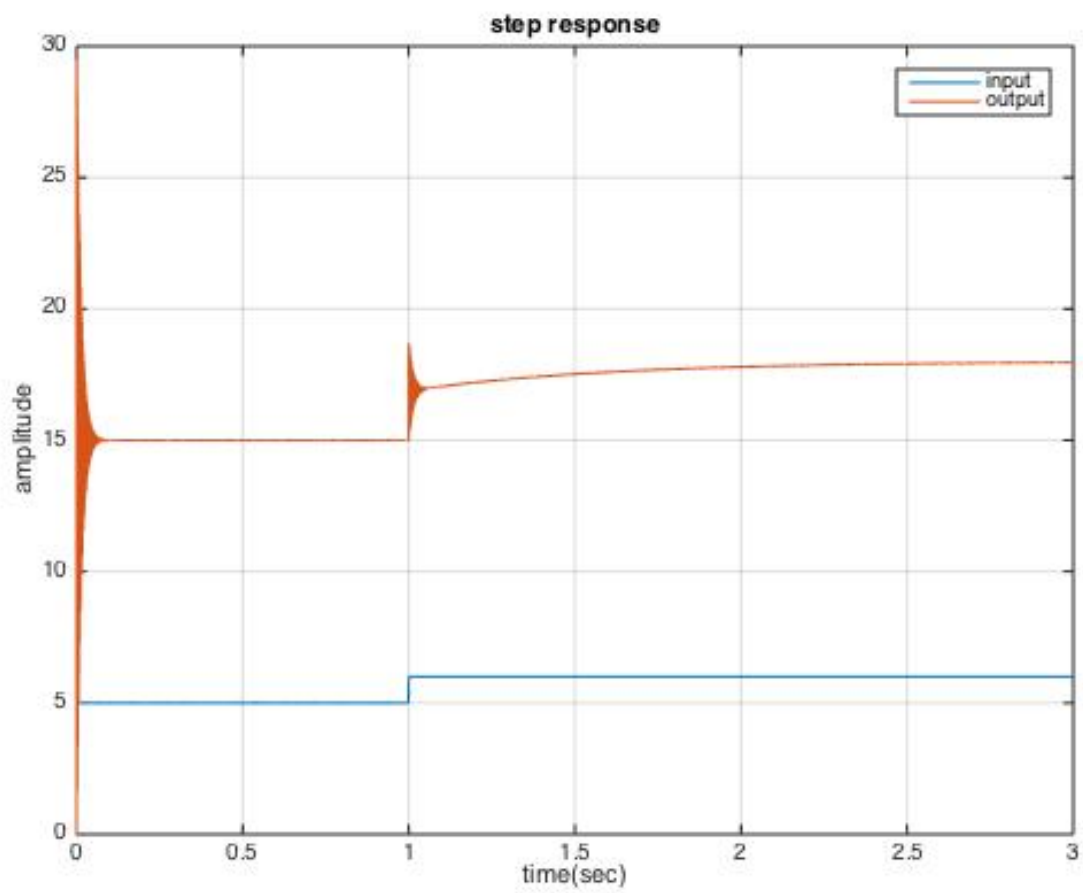

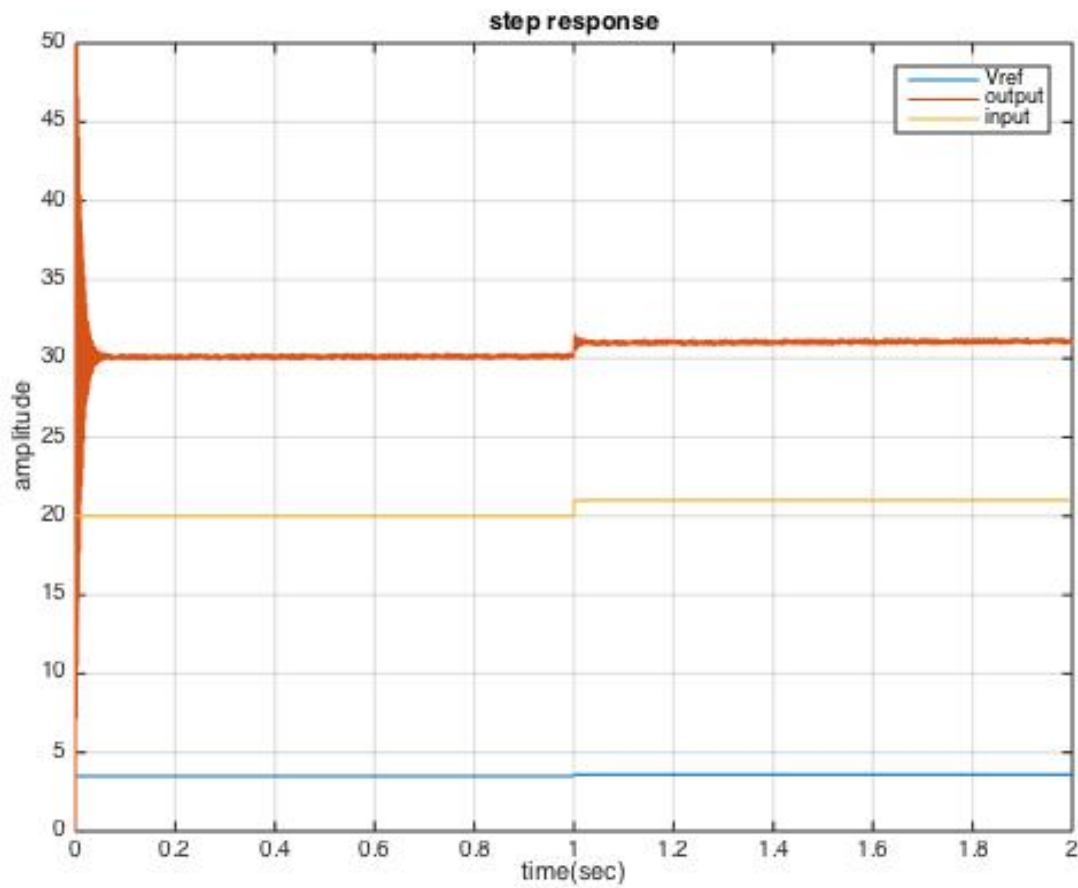

(u)

when $G_c(s)=1$, the damping is huge.
 when using PD controller as $G_c(s)$, the damping decrease.
 when using PID as $G_c(s)$, the settling time is quicker
 then using PD. Both of PD and PID reach the steady state.

2- A boost converter is used with the following parameters:

$$V = 20 \text{ v in}$$

$$L = 0.5 \text{ mH}$$

$$C = 500 \text{ }\mu\text{F}$$

$$f = 100 \text{ kHz s}$$

$$R = 10 \text{ }\Omega$$

The boost converter will be regulated using a feedback control similarly to questions 1.

The output voltage is desired to be 35 v . The available voltage on the board to be used as a reference voltage is 3.5 v , $V = 1$, assuming ideal components, m

- i) Repeat parts a)-l) similarly to question 1
- ii) Based on the system response and the bode plots, design a compensator to be used as $G_c(s)$
- iii) Show the system response for a small change in the reference voltage and a small change in the input voltage from both the simulated circuit and your $T(s)$ model with $G_c(s)$ being the designed compensator transfer function (while applying the feedback control).
- iv) Comment on the feedback control results.

Q2

1)

a).

$$H(s) = \frac{V_{ref}}{V_o} = \frac{3.5}{35} = \underline{\underline{0.1}}$$

b).

$$\frac{V_o}{V_i} = \frac{1}{1-D} = \frac{35}{20} \Rightarrow \underline{\underline{D = 0.429}}$$

c)

$$G_{Vo}(s) = \frac{G_{Vo}}{1 + s/Q\omega_o + (s/\omega_o)^2}$$

$$G_d(s) = \frac{G_{d0}(1 - s/\omega_z)}{1 + s/Q\omega_o + (s/\omega_o)^2}$$

$$G_{Vo} = \frac{1}{D} = 1.75$$

$$G_{d0} = \frac{V_o}{D} = 61.4$$

$$\omega_o = D'/\sqrt{LC} = 1140$$

$$Q = D'R\sqrt{C}/L = 5.7$$

$$\omega_z = D'^2 R/L = 6498$$


$$\Rightarrow G_{Vo}(s) = \frac{1.75}{1 + 1.54 \times 10^{-4} s + 7.69 \times 10^{-7} s^2}$$

$$G_d(s) = \frac{61.4 * (1 - 1.54 \times 10^{-4} s)}{1 + 1.54 \times 10^{-4} s + 7.69 \times 10^{-7} s^2}$$

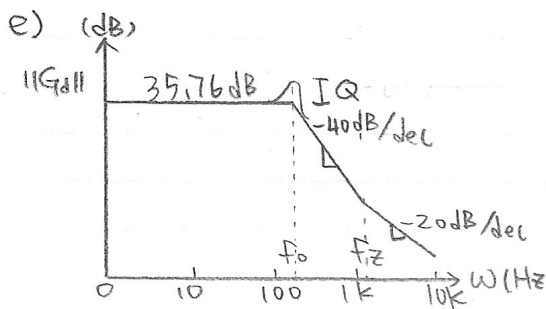2)

IV)

after applying the compensator, the system became a stable system.




$$G_{d0} = 61.4 \rightarrow 35.76 \text{ dB}$$

$$f_o = 181.44 \text{ Hz}$$

$$f_z = 1034.19 \text{ Hz}$$


$$Q = 5.7 \Rightarrow 15.12 \text{ dB}$$

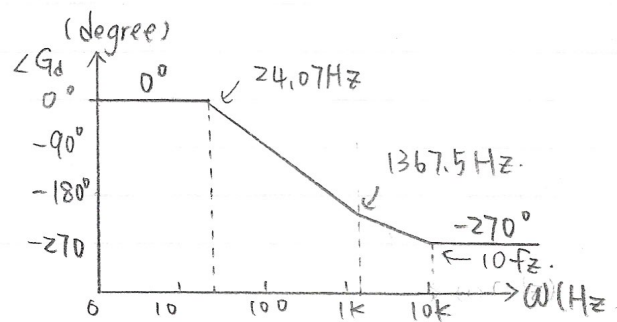

$$10^{-3} f_o = 24.07 \text{ Hz}$$

$$10^3 f_o = 1367.5 \text{ Hz}$$


$$10 f_z = 10341.9 \text{ Hz}$$

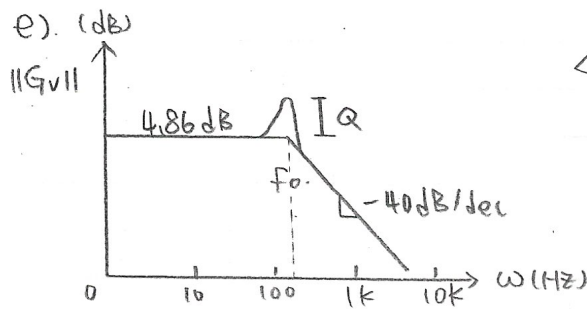

$$G_{v0} = 1.75 \rightarrow 4.86 \text{ dB}$$

$$f_0 = 181.44 \text{ Hz}$$


$$Q = 5.7 \rightarrow 15.12 \text{ dB}$$

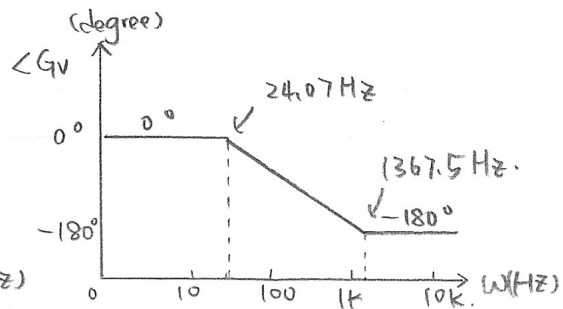

$$10^{-3} f_0 = 24.07 \text{ Hz}$$

$$10^3 f_0 = 1367.5 \text{ Hz}$$

f).

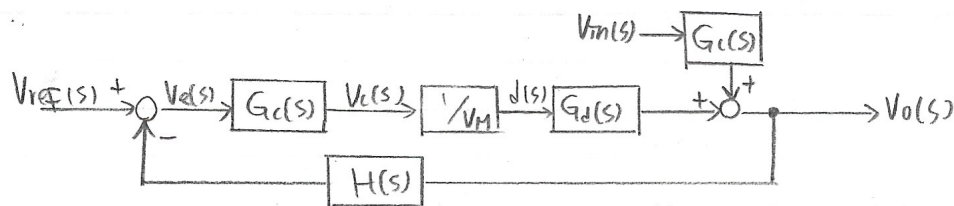


g).

$$T(s) = H(s) G_c(s) G_d(s) \frac{1}{V_m}$$

$$= 0.1 \times 1 \times \frac{61.4 (1 - 1.54 \times 10^{-4} s)}{1 + 1.54 \times 10^{-4} s + 7.69 \times 10^{-7} s^2} \times \frac{1}{1}$$

$$= \frac{61.4 (1 - 1.54 \times 10^{-4} s)}{1 + 1.54 \times 10^{-4} s + 7.69 \times 10^{-7} s^2}$$

h).

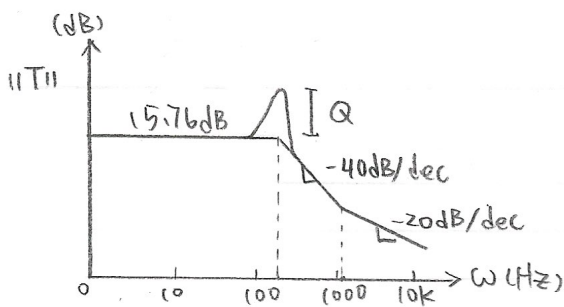


$$T_0 = 6.14 \rightarrow 15.76 \text{ dB}$$

$$f_0 = 181.44 \text{ Hz}$$

$$f_z = 1034 \text{ Hz}$$

$$Q = 5.7 \rightarrow 15.12 \text{ dB}$$

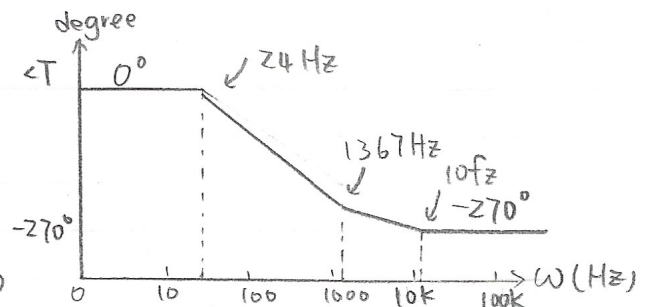

$$10^{-3} f_0 = 24.07 \text{ Hz}$$

$$10^3 f_0 = 1367.5 \text{ Hz}$$

$$10 f_z = 10340 \text{ Hz}$$

(i)

$T(s)$'s Bode plot looks similar with $G_d(s)$
But they have different DC gain.

(j)

By using MATLAB Function, we can get the crossover
frequency = 3.19×10^3 Hz . $\phi_m = -22.0518^\circ$

(k)

when $G_d(s)$ has zero at ω_z that makes the system an
unstable system \rightarrow cannot get the output response and inductor
current.

(l)

Same result as (k)

```
>> H=0.1;  
>> Gc=1;  
>> Gd=tf([61.4*(-1.54e-4) 61.4],[7.69e-7 1.54e-4 1]);  
>> Vm=1;  
>> T=H*Gc*Gd/Vm;  
>> bode(T)  
>> [Gm,Pm,Wgm,Wpm] = margin(T)  
Warning: The closed-loop system is unstable.  
> In warning at 25  
In DynamicSystem.margin at 65
```

Gm =

0.1629

Pm =

-22.0518

Wgm =

1.6127e+03

Wpm =

3.1906e+03

