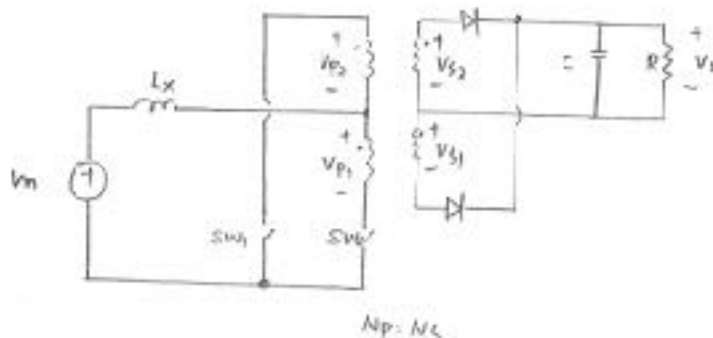


The current fed converter in the figure shown below has the following parameters.  $V = 24 \text{ V}$ ,  $N_p/N_s = 2$ ,  $R = 10 \Omega$ , and  $D = 0.35$ . Assuming that the input inductor is very large, determine the following:

- a) The output voltage and the input current.
- b) The maximum voltage across every switch.



$$V_{in} = 24 \text{ V}$$

$$N_p/N_s = 2$$


$$R = 10 \Omega$$

$$D = 0.35$$

$$f_s = 10 \text{ kHz}$$

$$L_x = 10 \text{ mH}$$


① SW<sub>1</sub> ON, SW<sub>2</sub> OFF.

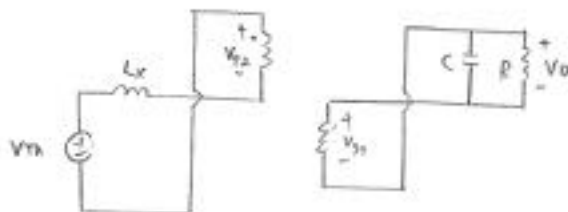

$$V_{Lx} = V_s + V_{p2}$$

$$V_{p2} = V_o \cdot \frac{N_p}{N_s}$$


② SW<sub>1</sub> OFF, SW<sub>2</sub> ON.

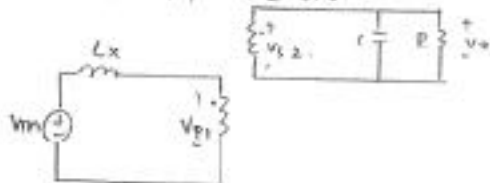

$$V_{Lx} = V_s - V_{p1}$$

$$V_{p1} = V_o \cdot \frac{N_p}{N_s}$$

③ Both ON.

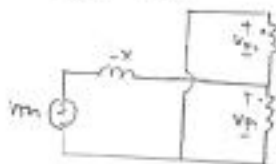

$$V_{Lx} = V_s$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{1}{2(1-D)} \cdot \frac{N_s}{N_p}$$

$$V_{SW1 \text{ max}} = V_{p1}$$

$$V_{SW2 \text{ max}} = V_{p2}$$

$$V_{SW1, max} = V_{p1} = V_o \frac{N_D}{N_S} = \underline{\underline{34,286V}}$$

$$V_{SW2, max} = V_{p2} = V_o \frac{N_p}{N_S} = \underline{\underline{34,286V}}$$

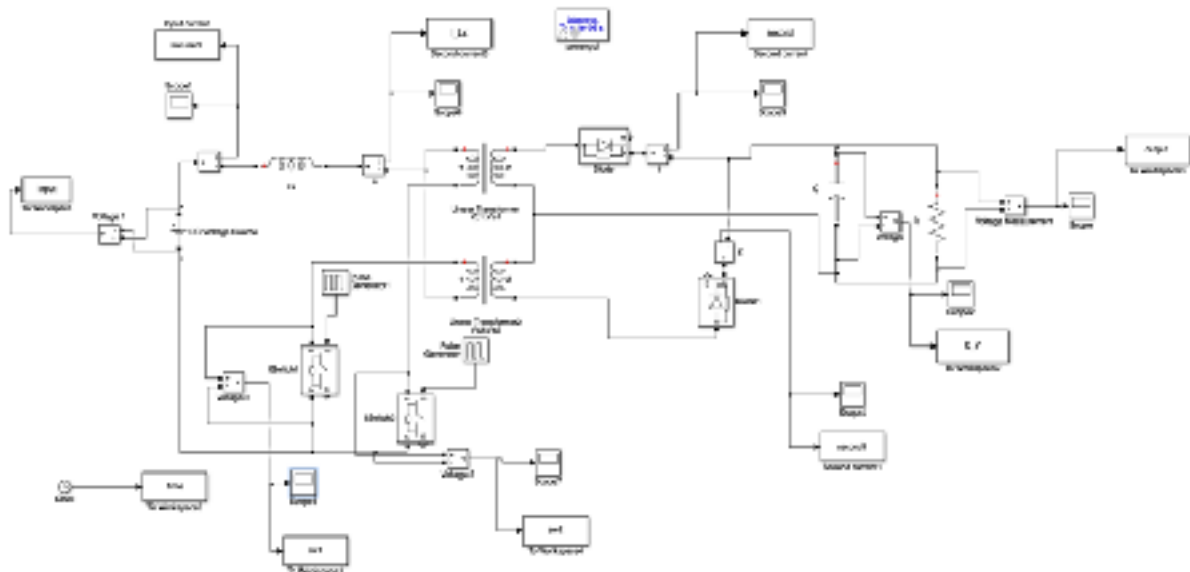


fig1. simulation of current fed converter