

A Cuk converter is used with the following parameters:

$$V = 12 \text{ V in}$$

$$D = 0.6$$

$$L_1 = 1 \text{ mH}$$

$$L_2 = 2 \text{ mH}$$

$$C_1 = 25 \mu\text{F}$$


$$C_2 = 5 \mu\text{F}$$

$$f = 50 \text{ kHz s}$$

$$P = 40 \text{ W}$$

Find the output voltage, the inductor current ripples (for both L_1 & L_2) and the capacitor

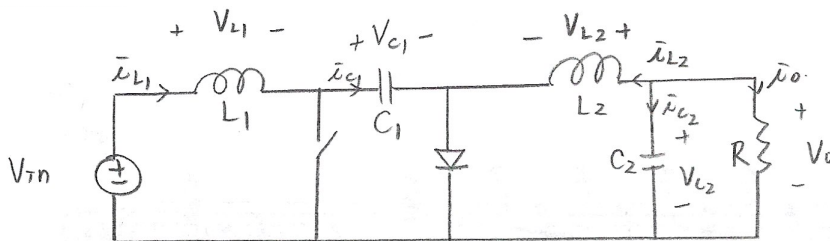Assuming ideal components, voltage ripples (for both C_1 & C_2).



$$V_{in} = 12 \text{ V}$$

$$D = 0.6$$

$$L_1 = 1 \text{ mH} \quad C_1 = 25 \mu\text{F}$$

$$L_2 = 2 \text{ mH} \quad C_2 = 5 \mu\text{F}$$

$$f_s = 50 \text{ kHz}$$

$$P = 40 \text{ W}$$

$$\frac{V_o}{V_i} = \frac{-D}{1-D} \Rightarrow V_o = \frac{-0.6}{(1-0.6)} \cdot 12 = \underline{\underline{-18 \text{ V}}}$$

$$\Delta \bar{I}_{L1} = \frac{V_i D}{f_s L_1} = \frac{12 \cdot 0.6}{(50 \times 10^3) (1 \times 10^{-3})} = \underline{\underline{0.144 \text{ A}}}$$

$$\Delta \bar{I}_{L2} = \frac{V_i D}{f_s L_2} = \frac{12 \cdot 0.6}{(50 \times 10^3) (2 \times 10^{-3})} = \underline{\underline{0.072 \text{ A}}}$$

$$\frac{\Delta V_{C2}}{V_o} = \frac{(1-D)}{8 L_2 f_s^2 \cdot C_2} = \frac{(1-0.6)}{8 \cdot (2 \times 10^{-3}) (50 \times 10^3)^2 \cdot (5 \times 10^{-6})} = \underline{\underline{2 \times 10^{-3}}}$$

$$\Delta Q_1 = C_1 \Delta V_{C1} = \Delta t \Delta \bar{I}_{C1} = I_{L1} (1-D) T$$

$$I_{L1} = I_{L2} = \frac{-D}{1-D} \cdot I_o = \frac{-D}{1-D} \cdot \frac{P}{V_o} = 3.33$$

$$\Rightarrow \Delta V_{C1} = \frac{I_{L1} (1-D) T}{C_1} = \frac{3.33 (1-0.6)}{(50 \times 10^3) \cdot (25 \times 10^{-6})} = \underline{\underline{1.0656 \text{ V}}}$$

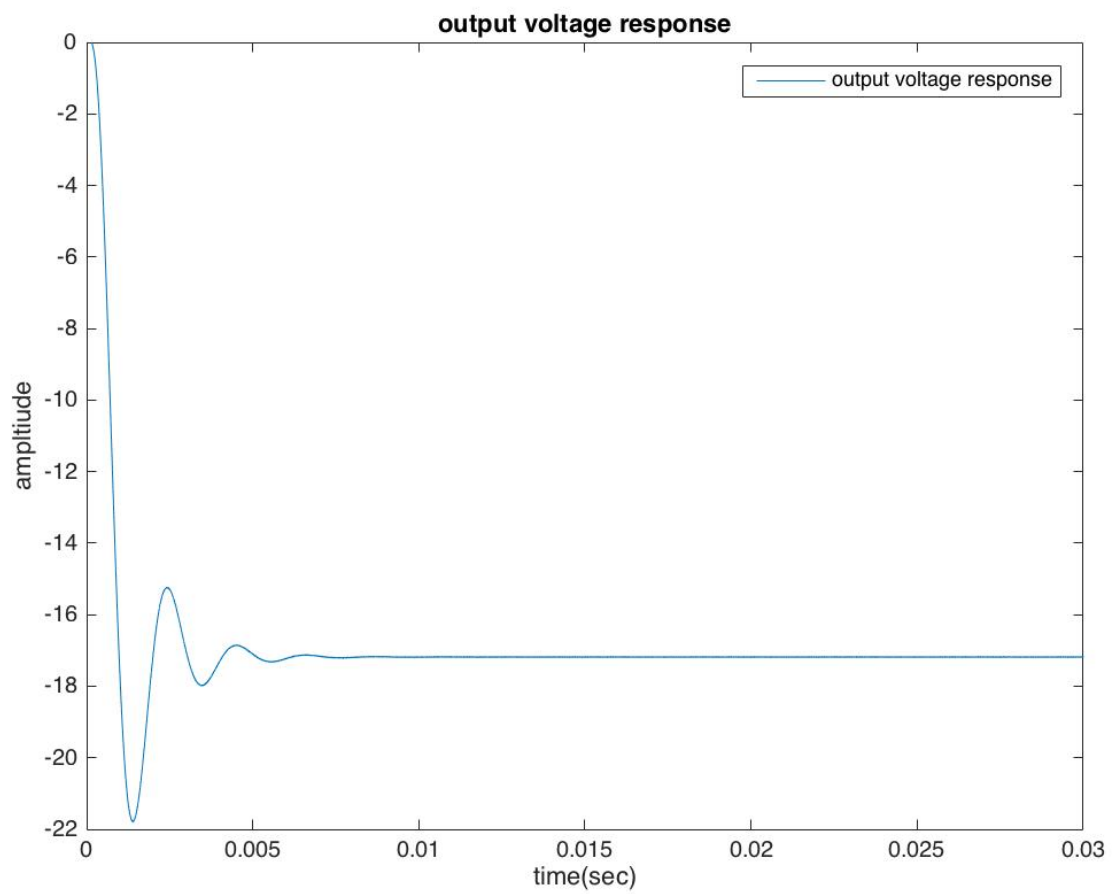


Figure 1. Output voltage waveform.

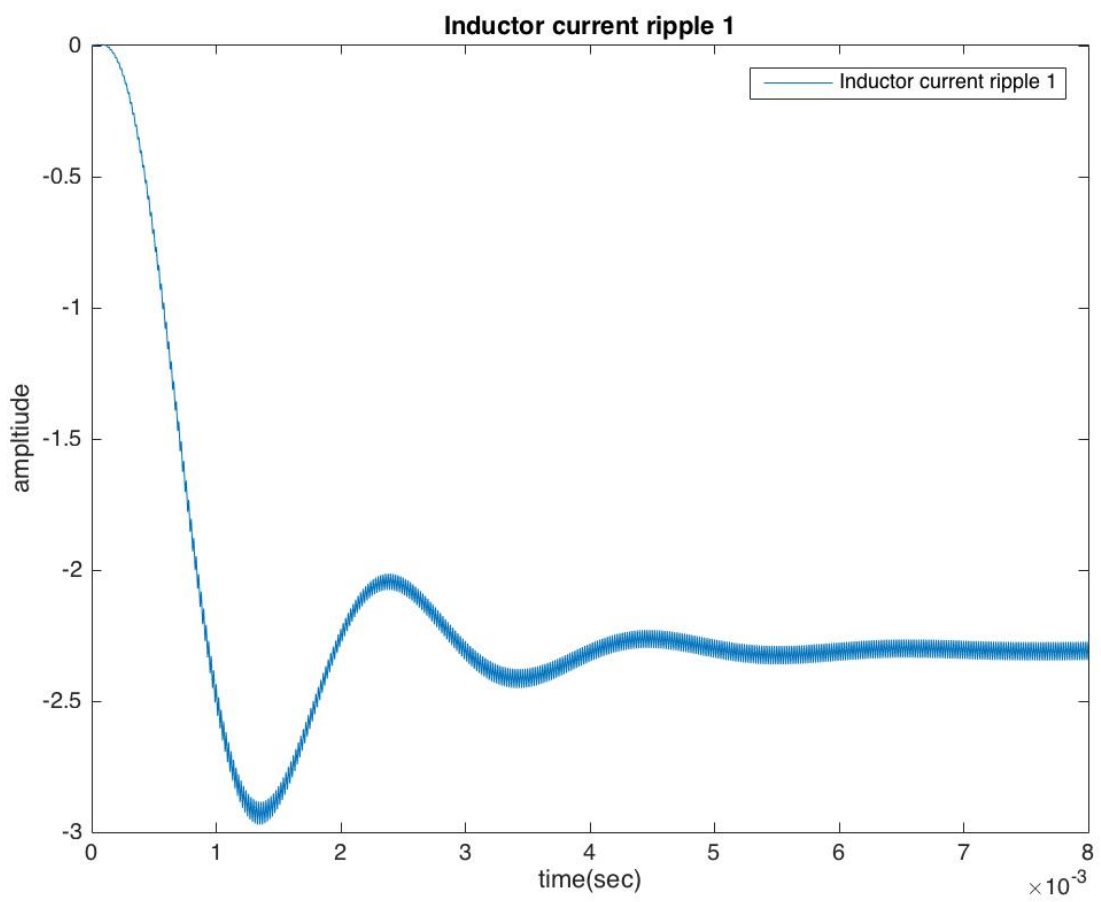
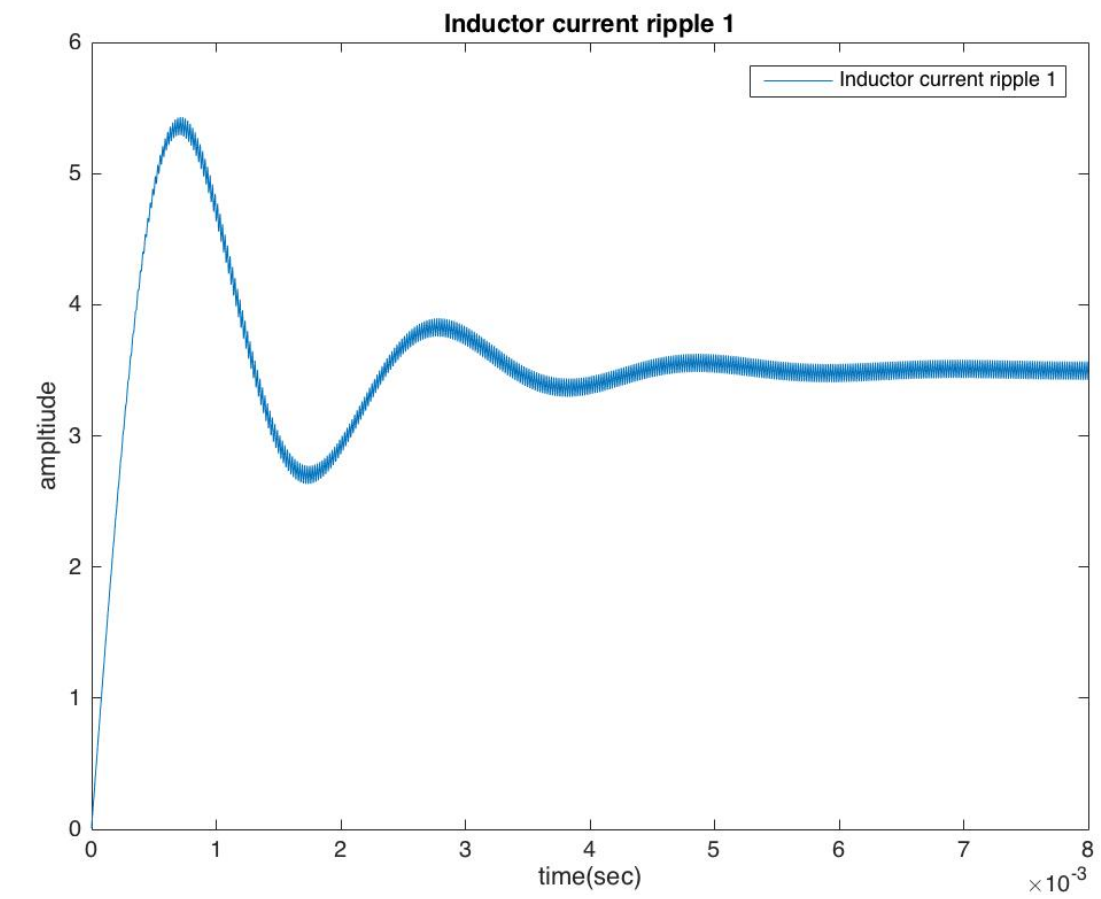


Figure 2. Inductor current waveform.

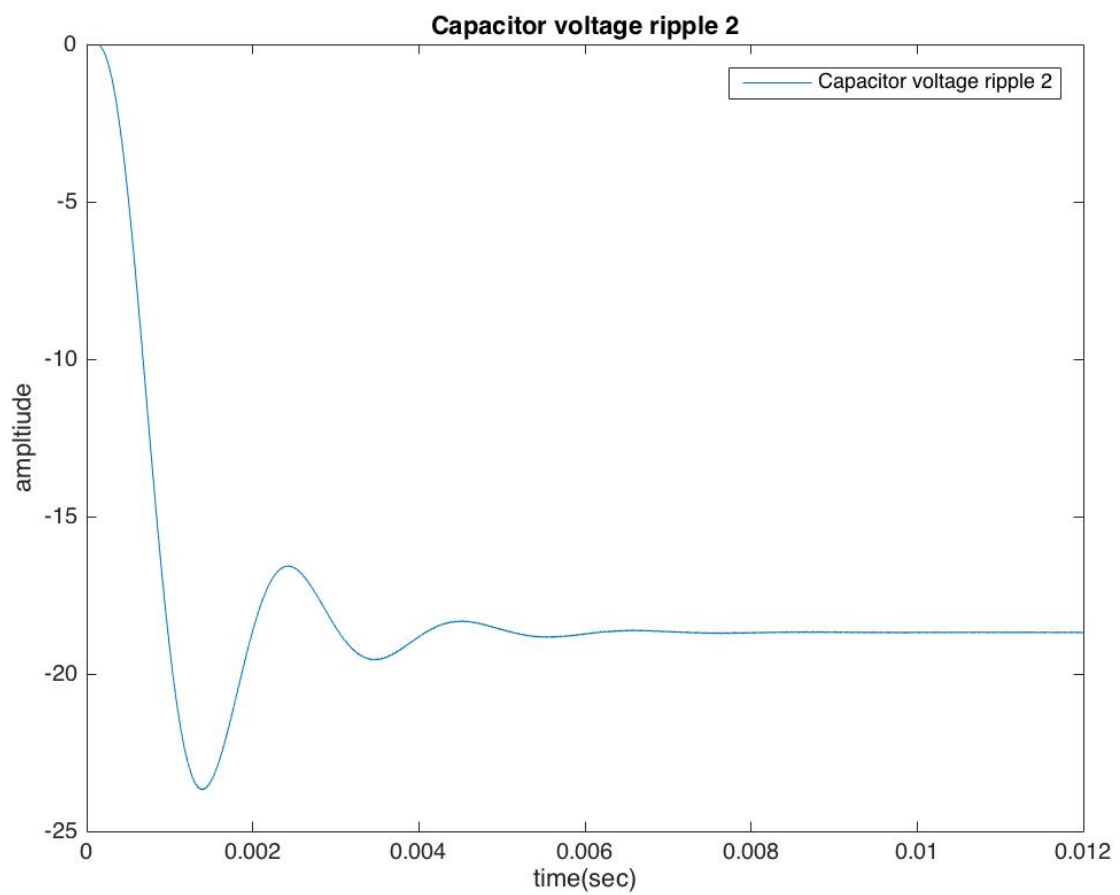
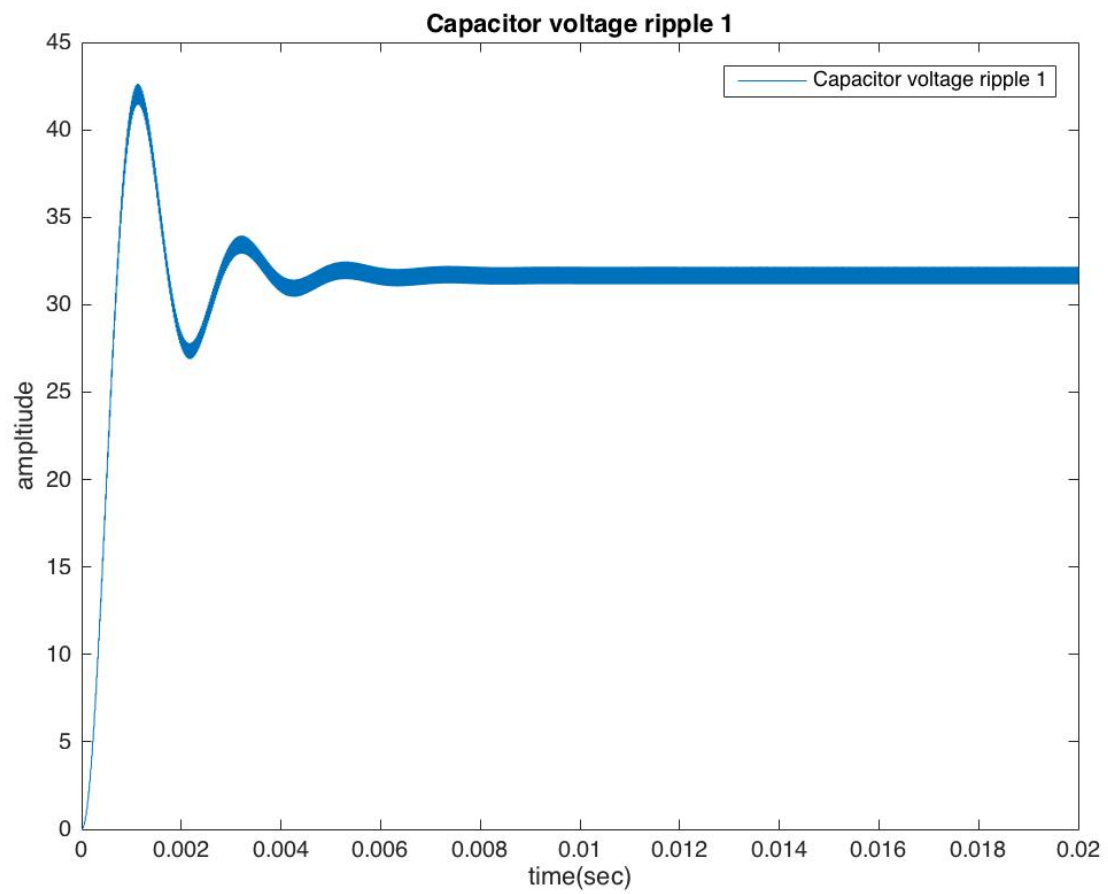


Figure 3. Capacitor voltage waveform.

(c)

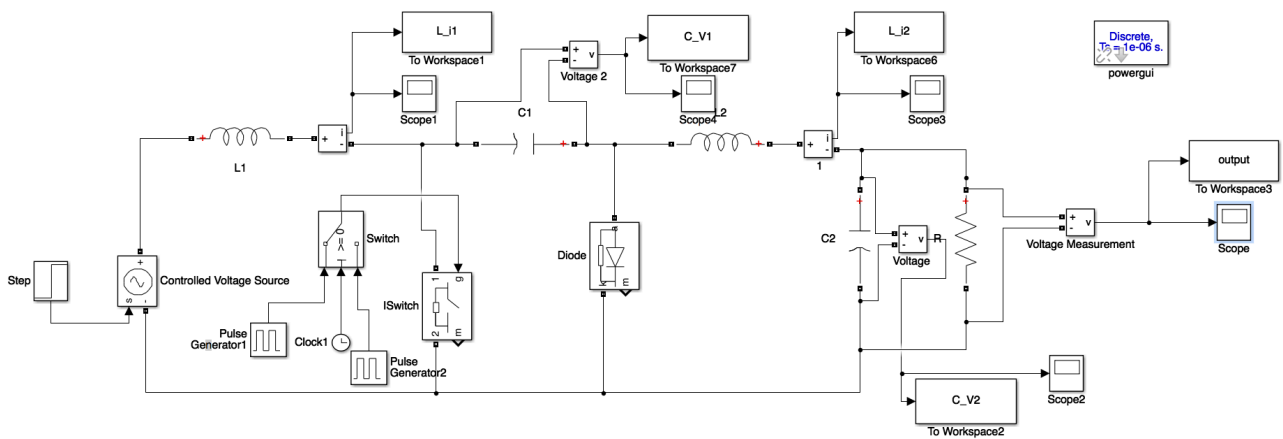


Figure 4. MATLAB Simulink model.


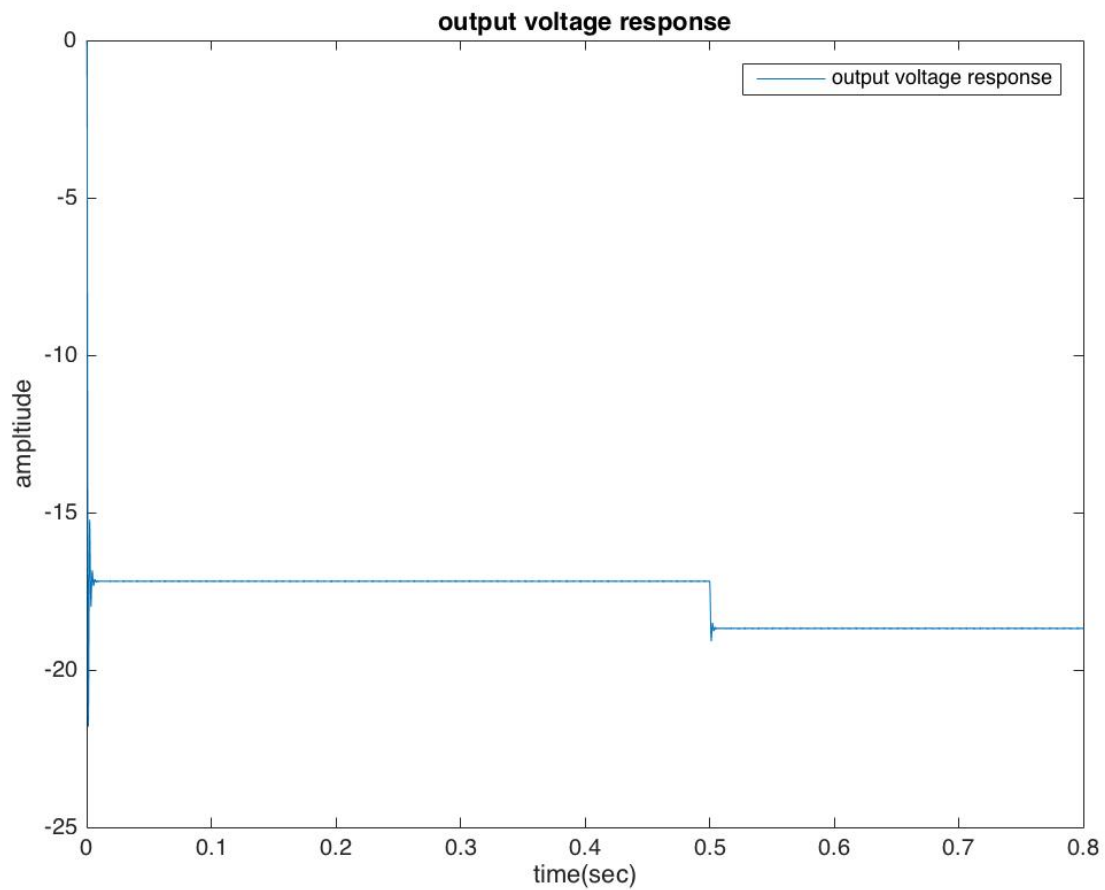


Figure 5. Output voltage response.

(d) Use state space.

① ON.

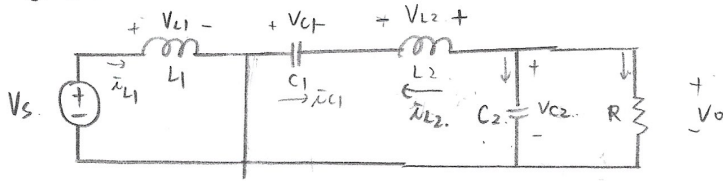

$$x = \begin{bmatrix} \hat{x}_{L1} \\ \hat{x}_{L2} \\ v_{C1} \\ v_{C2} \end{bmatrix}$$

$$u = [V_s]$$

$$y = [V_o]$$

$$V_s = V_{L1} = L_1 \dot{\hat{x}}_{L1}$$

$$V_{L2} = V_{C1} - V_{C2} = L_2 \dot{\hat{x}}_{L2}$$

$$\hat{x}_{C1} = -\hat{x}_{L2} = C_1 \dot{V}_{C1}$$


$$\hat{x}_{C2} = C_2 \dot{V}_{C2} = \hat{x}_{L2} - \hat{x}_o = \hat{x}_{L2} - \frac{V_{C2}}{R}$$

$$V_o = V_{C2}$$

$$\dot{\hat{x}} = \begin{bmatrix} \hat{x}_{L1} \\ \hat{x}_{L2} \\ \hat{x}_{C1} \\ \hat{x}_{C2} \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{L_2} & -\frac{1}{L_2} \\ 0 & -\frac{1}{C_1} & 0 & 0 \\ 0 & \frac{1}{C_2} & 0 & -\frac{1}{RC_2} \end{bmatrix} \begin{bmatrix} \hat{x}_{L1} \\ \hat{x}_{L2} \\ v_{C1} \\ v_{C2} \end{bmatrix} + \begin{bmatrix} \frac{1}{L_1} \\ 0 \\ 0 \\ 0 \end{bmatrix} [V_s]$$

$$y = [V_o] = [0 \ 0 \ 0 \ 1] \begin{bmatrix} \hat{x}_{L1} \\ \hat{x}_{L2} \\ v_{C1} \\ v_{C2} \end{bmatrix}$$

② off.

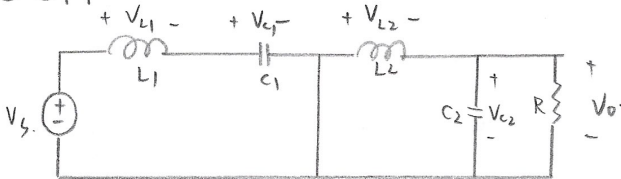

$$V_{L1} = V_s - V_{C1} = L_1 \dot{\hat{x}}_{L1}$$

$$V_{L2} = -V_{C2} = L_2 \dot{\hat{x}}_{L2}$$

$$\hat{x}_{C1} = \hat{x}_{L1} = C_1 \dot{V}_{C1}$$

$$\hat{x}_{C2} = \hat{x}_{L2} - \hat{x}_o = \hat{x}_{L2} - \frac{V_{C2}}{R} = C_2 \dot{V}_{C2}$$

$$V_o = V_{C2}$$

$$\dot{\hat{x}} = \begin{bmatrix} 0 & 0 & \frac{-1}{L_1} & 0 \\ 0 & 0 & 0 & \frac{-1}{L_2} \\ \frac{1}{C_1} & 0 & 0 & 0 \\ 0 & \frac{1}{C_2} & 0 & -\frac{1}{RC_2} \end{bmatrix} \begin{bmatrix} \hat{x}_{L1} \\ \hat{x}_{L2} \\ v_{C1} \\ v_{C2} \end{bmatrix} + \begin{bmatrix} \frac{1}{L_1} \\ 0 \\ 0 \\ 0 \end{bmatrix} [V_s]$$

$$y = [0 \ 0 \ 0 \ 1] \begin{bmatrix} \hat{x}_{L1} \\ \hat{x}_{L2} \\ v_{C1} \\ v_{C2} \end{bmatrix}$$

$$\begin{cases} \dot{\bar{x}} = (A_1 d + A_2 d') \bar{x} + (B_1 d + B_2 d') \bar{u} \\ \bar{y} = (C_1 d + C_2 d') \bar{x} + (D_1 d + D_2 d') \bar{u} \end{cases}$$

$$\Rightarrow A_v = \begin{bmatrix} 0 & 0 & \frac{-d'}{L_1} & 0 \\ 0 & 0 & \frac{d}{L_2} & \frac{-1}{L_2} \\ \frac{d}{C_1} & -\frac{d}{C_1} & 0 & 0 \\ 0 & \frac{1}{C_2} & 0 & \frac{-1}{RC_2} \end{bmatrix}$$

$$B_v = \begin{bmatrix} \frac{1}{L_1} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$C_v = \begin{bmatrix} 0 & 0 & 0 & 1 \end{bmatrix}$$

$$TF = C_v (sI - A_v)^{-1} B_v = \frac{10^{14} \times (-9.6)}{10^{14} (0.0034s + 6.4)} = \frac{-9.6}{0.0034s + 6.4}$$